
LLC Resonant Converter

Infinite Technologies




Content

- LLC Topology
 - Benefits and Drawbacks
 - Basic Analysis of LLC Converter
 - Modes of Operation
 - Design
- ICE2HS01G Resonant Mode Controller
 - Key Features
 - Protection
 - Design
- Reference Designs and Experimental Results
 - Solar LLC Converter
 - SMPS LLC Converter

3 LLC Benefits and Drawbacks vs. Phase Shift Full Bridge


LLC	Phase Shift Full Bridge
■ Benefits	
Full resonant → less EMI	Quasi resonant
Soft switching in primary and secondary sides → High efficiency	Secondary side is hard switching
Soft switching over a wide load range → High efficiency at light load	Soft switching is load dependent
No output inductor → Low BoM cost in magnetics	Needs one or two output inductors
Lower blocking voltage for secondary rectifiers → Lower cost, better FoM devices	Needs higher voltage devices
Half Bridge LLC and Full Bridge LLC covers wide power range applications.	More suitable for high power application
■ Drawbacks	
More Challenging control and design – knowledge intensive; integrated magnetics require sophisticated design approach	Easy control and straight forward design
Non trapezoidal current waveform → Higher conduction loss overcome by lower Ron FETs, with lower FOM	trapezoidal current waveform → Lower conduction loss
Variable frequency to regulate output voltage	Fixed frequency control

Concept of LLC Resonant Converter

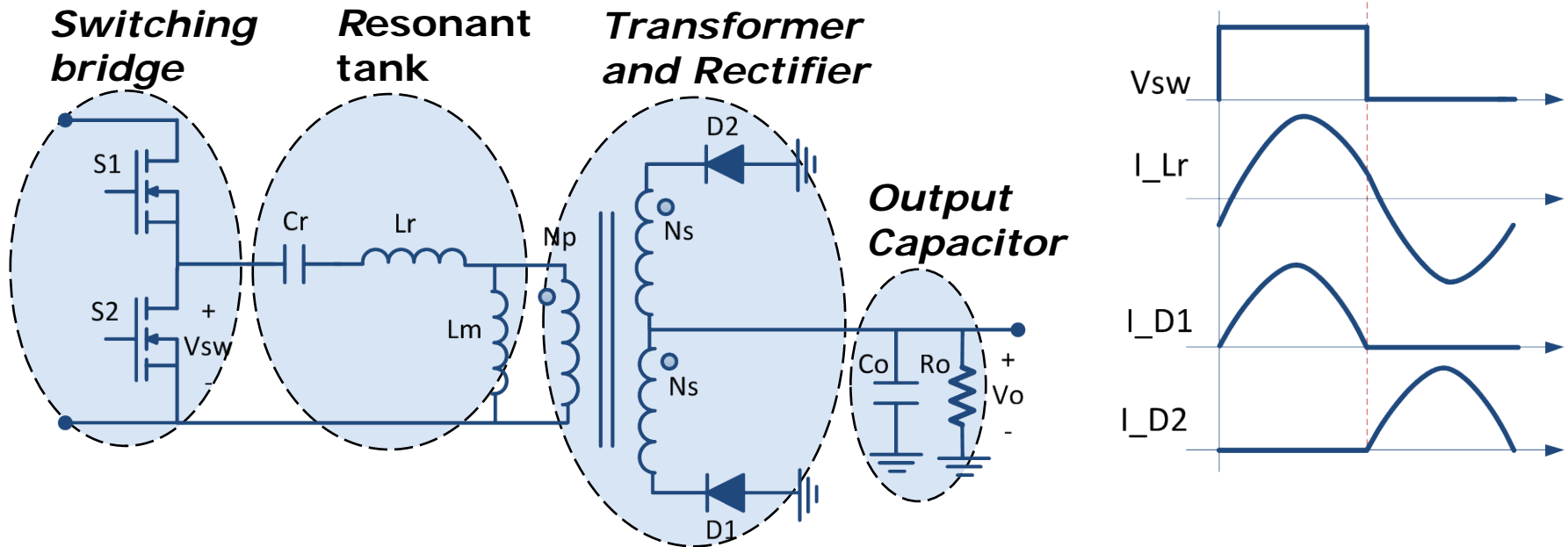


Switching bridge generates square waveform to excite **resonant tank**, resonant sinusoidal current gets scaled and rectified by **transformer and rectifier**, **output capacitor** filters the ac current to output DC voltage

Basic Analysis of LLC Converter

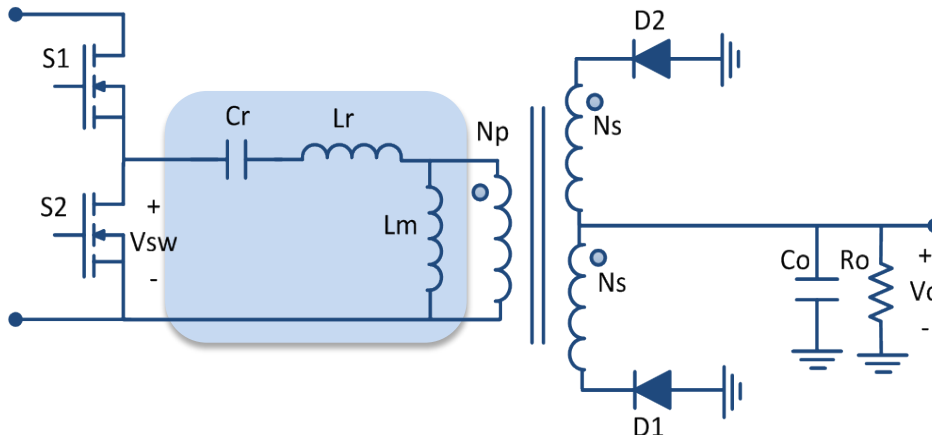

Equivalent circuit

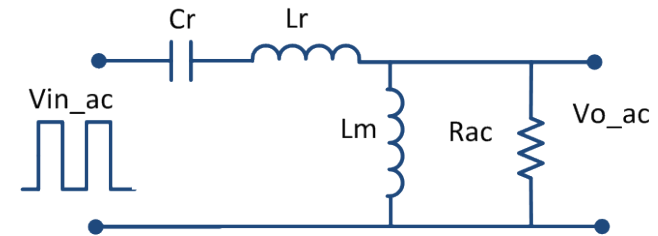


$$K(Q, m, Fx) = \frac{V_{o_ac}}{V_{in_ac}} = \frac{Fx^2(m-1)}{\sqrt{(m \cdot Fx^2 - 1)^2 + Fx^2 \cdot (Fx^2 - 1)^2 \cdot (m-1)^2 \cdot Q^2}}$$

$$G = \frac{V_o}{V_{in}} = \frac{1}{2} \cdot K(Q, m, Fx) \cdot \frac{N_s}{N_p}$$


$$Fx = \frac{f_s}{f_r} \quad f_r = \frac{1}{2\pi\sqrt{L_r C_r}} \quad Q = \frac{\sqrt{L_r/C_r}}{R_{ac}} \quad R_{ac} = \frac{8}{\pi^2} \cdot \frac{N_p^2}{N_s^2} \cdot R_o \quad m = \frac{L_r + L_m}{L_r}$$

Basic Analysis of LLC Converter
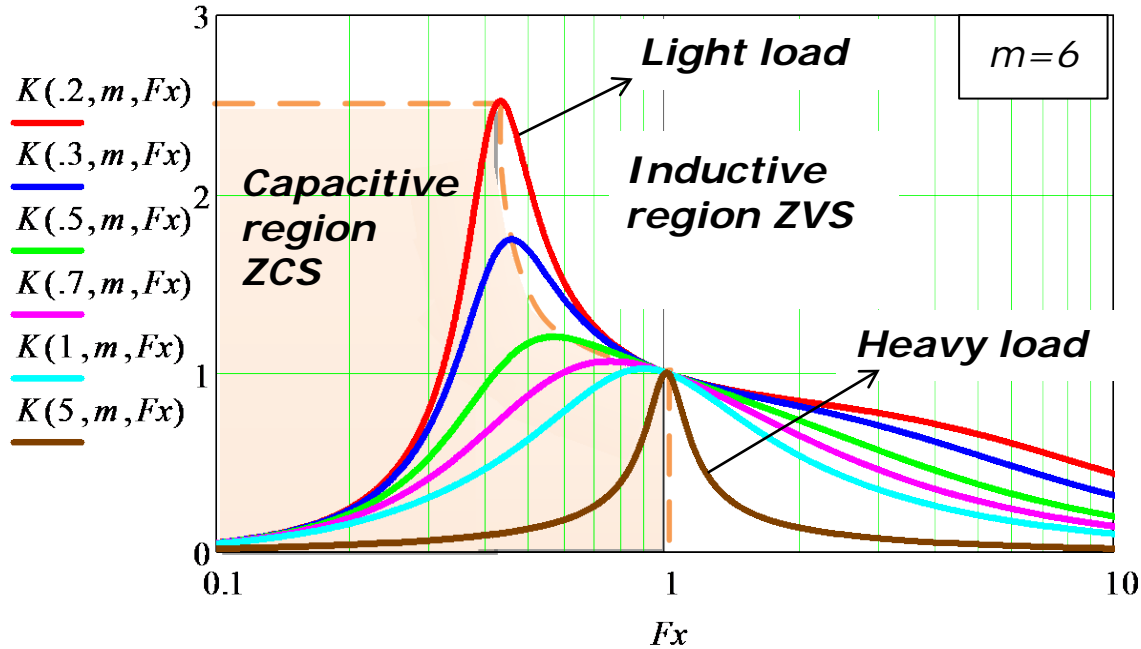
$$K(Q, m, Fx) = \frac{V_{o_ac}}{V_{in_ac}} = \frac{Fx^2(m-1)}{\sqrt{(m \cdot Fx^2 - 1)^2 + Fx^2 \cdot (Fx^2 - 1)^2 \cdot (m-1)^2 \cdot Q^2}}$$



Modes of Operation

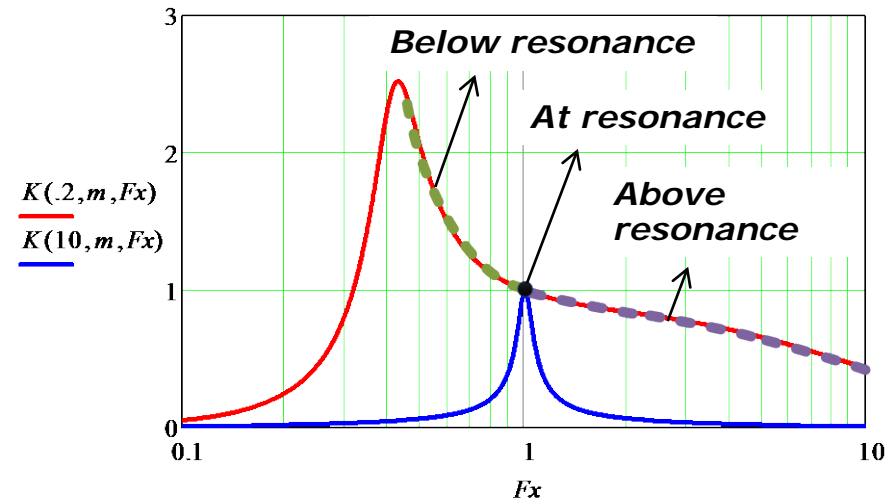

■ At resonance operation $f_s = f_r$

- Unity gain
- Optimal operational point




■ Below resonance operation $f_s < f_r$

- Boost gain
- Increased primary side conduction losses
- Has the risk of capacitive mode operation




■ Above resonance operation $f_s > f_r$

- Buck gain
- Increased Primary side turn off losses
- Reverse recovery for secondary side diodes
- Gain is less sensitive to frequency modulation



At Resonance Operation $f_s = f_r$

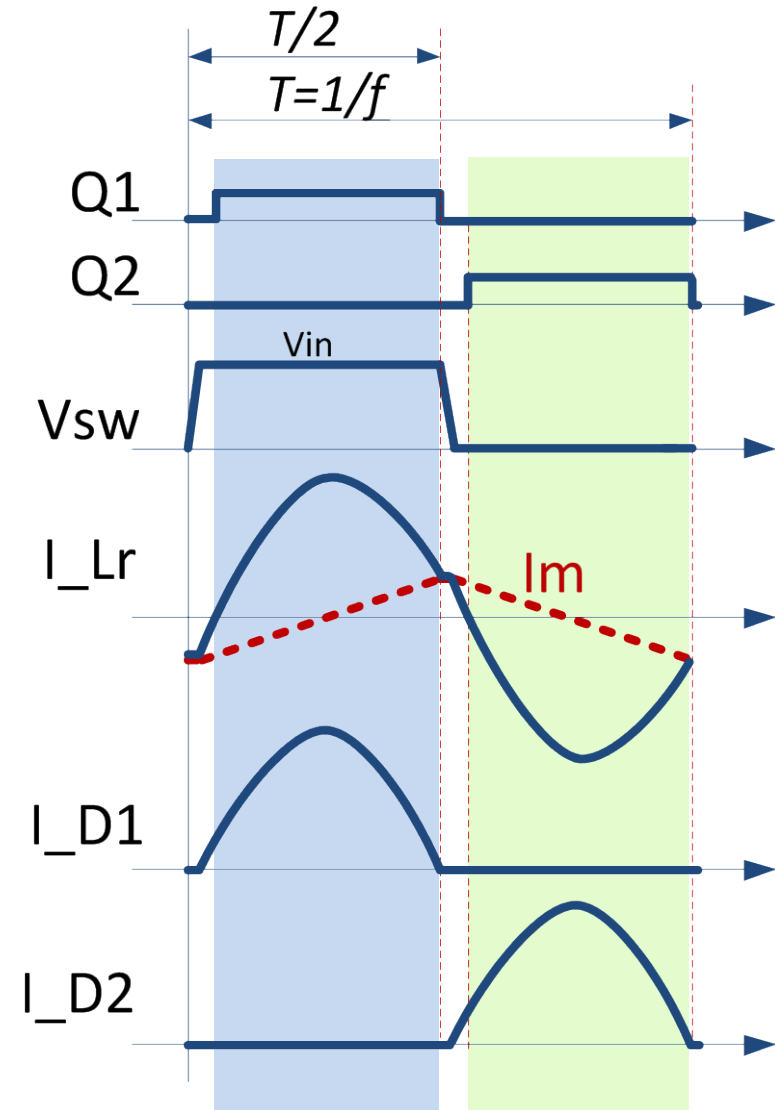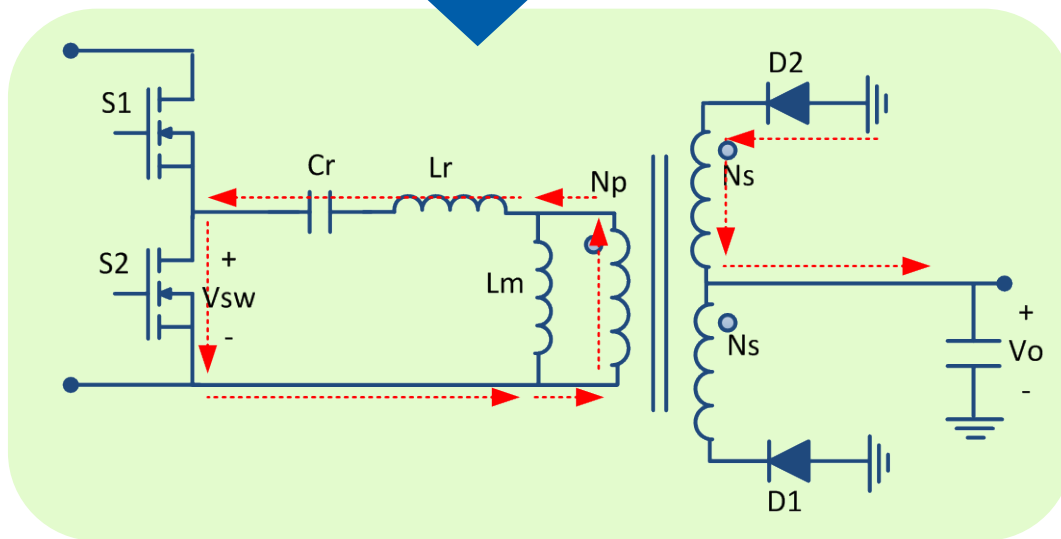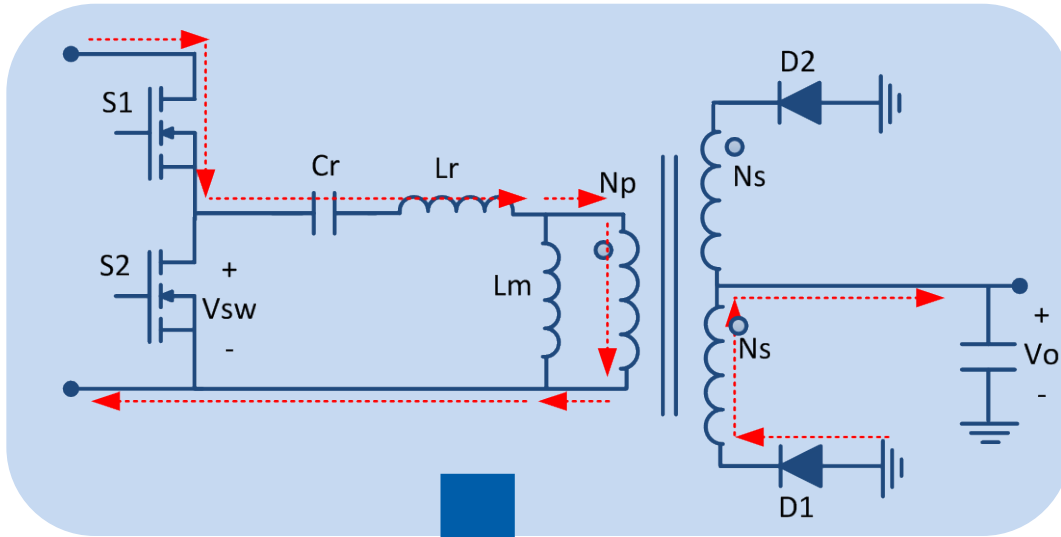




Above Resonance Operation $f_s > f_r$

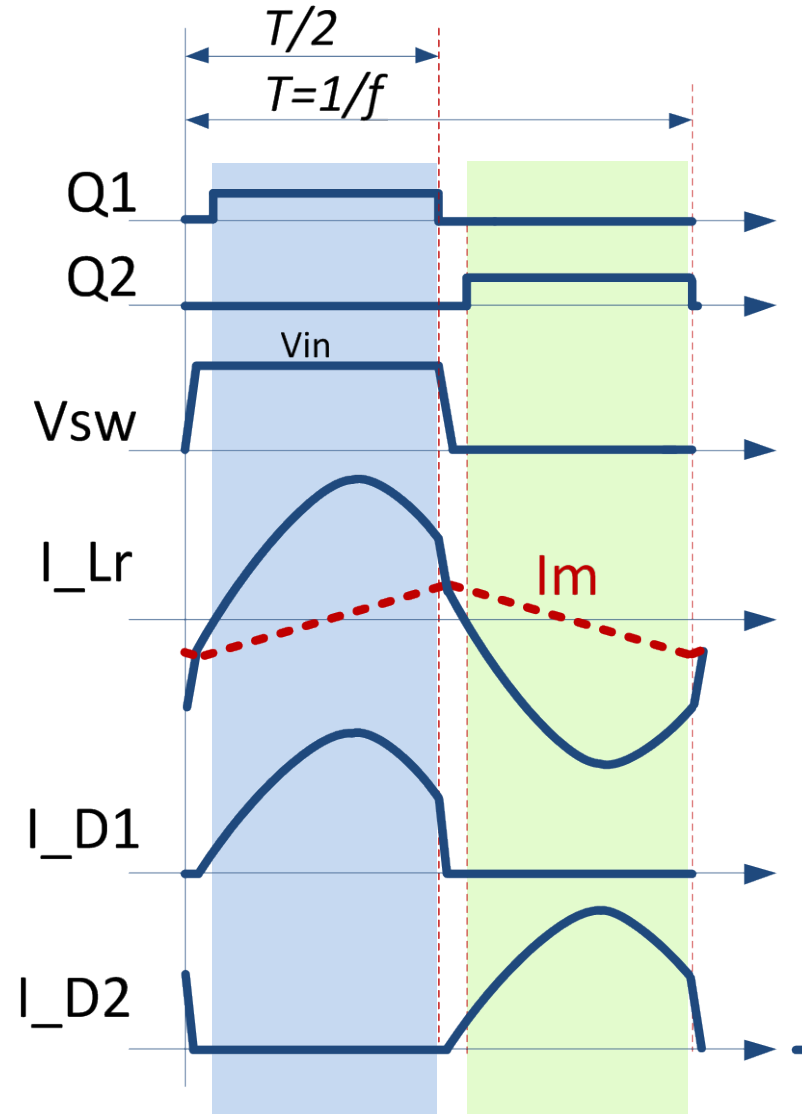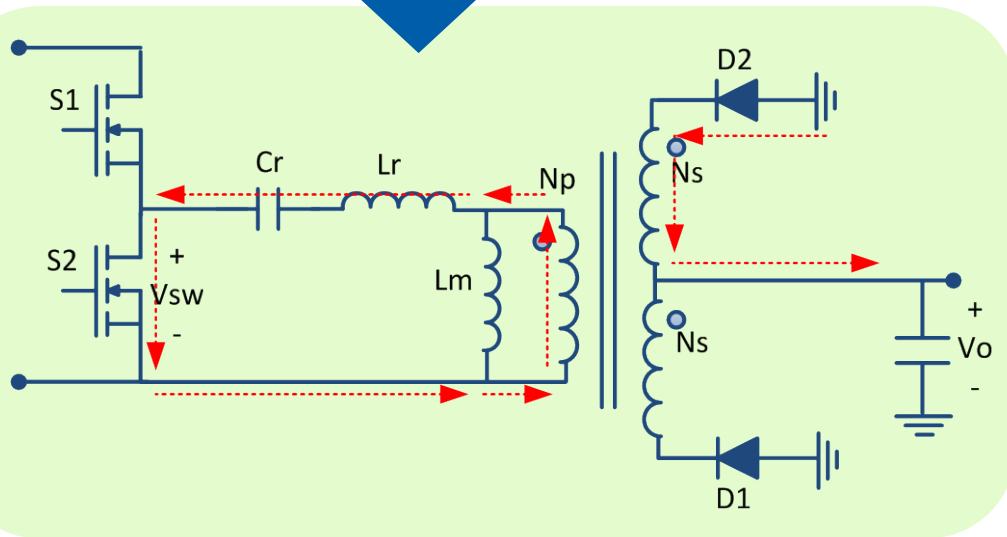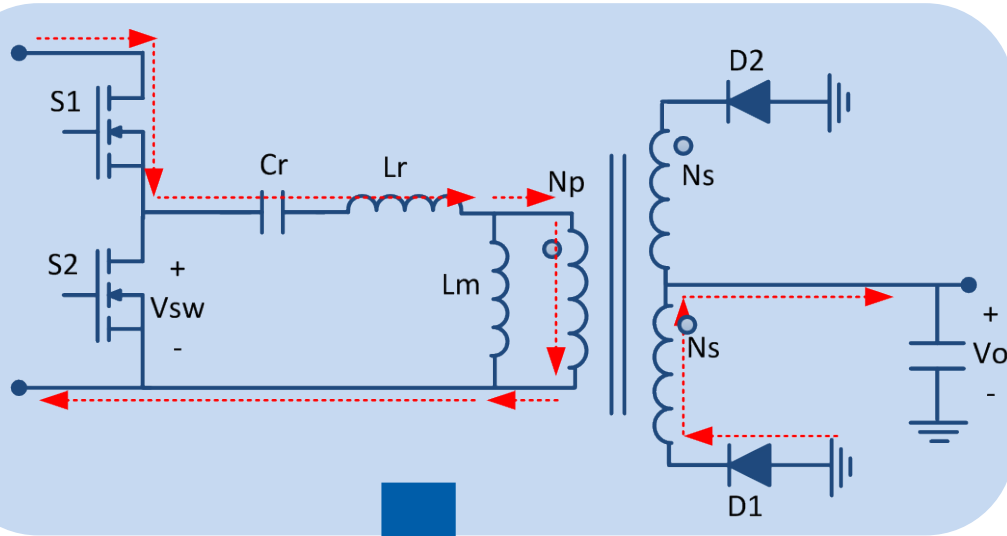

Below Resonance Operation $f_s < f_r$

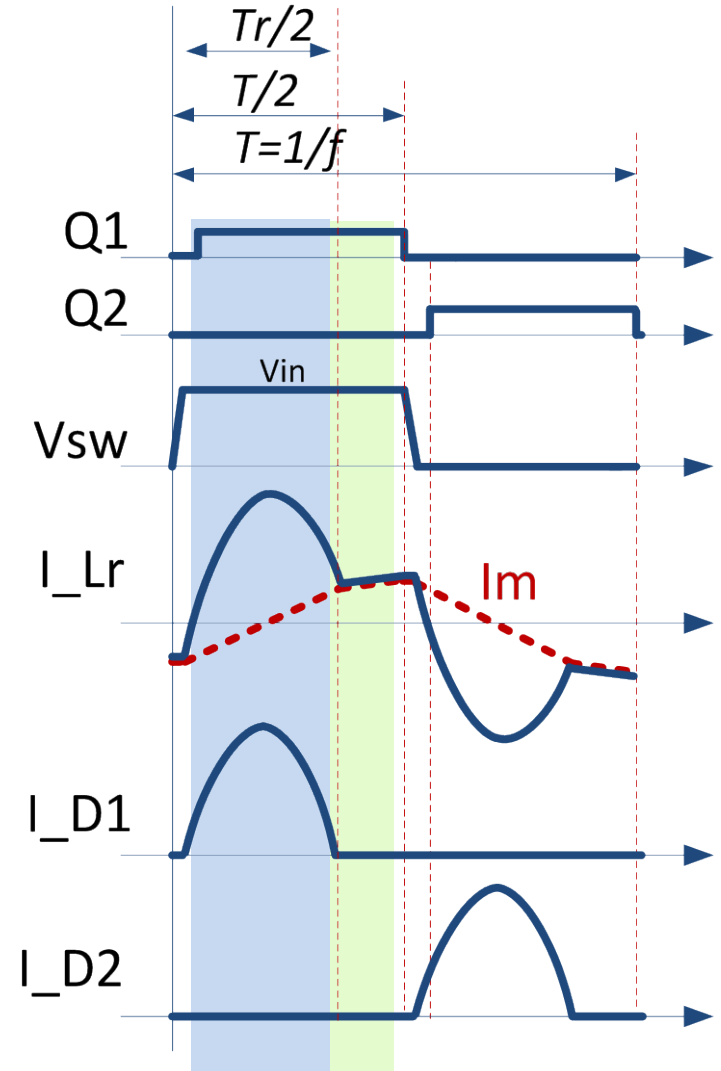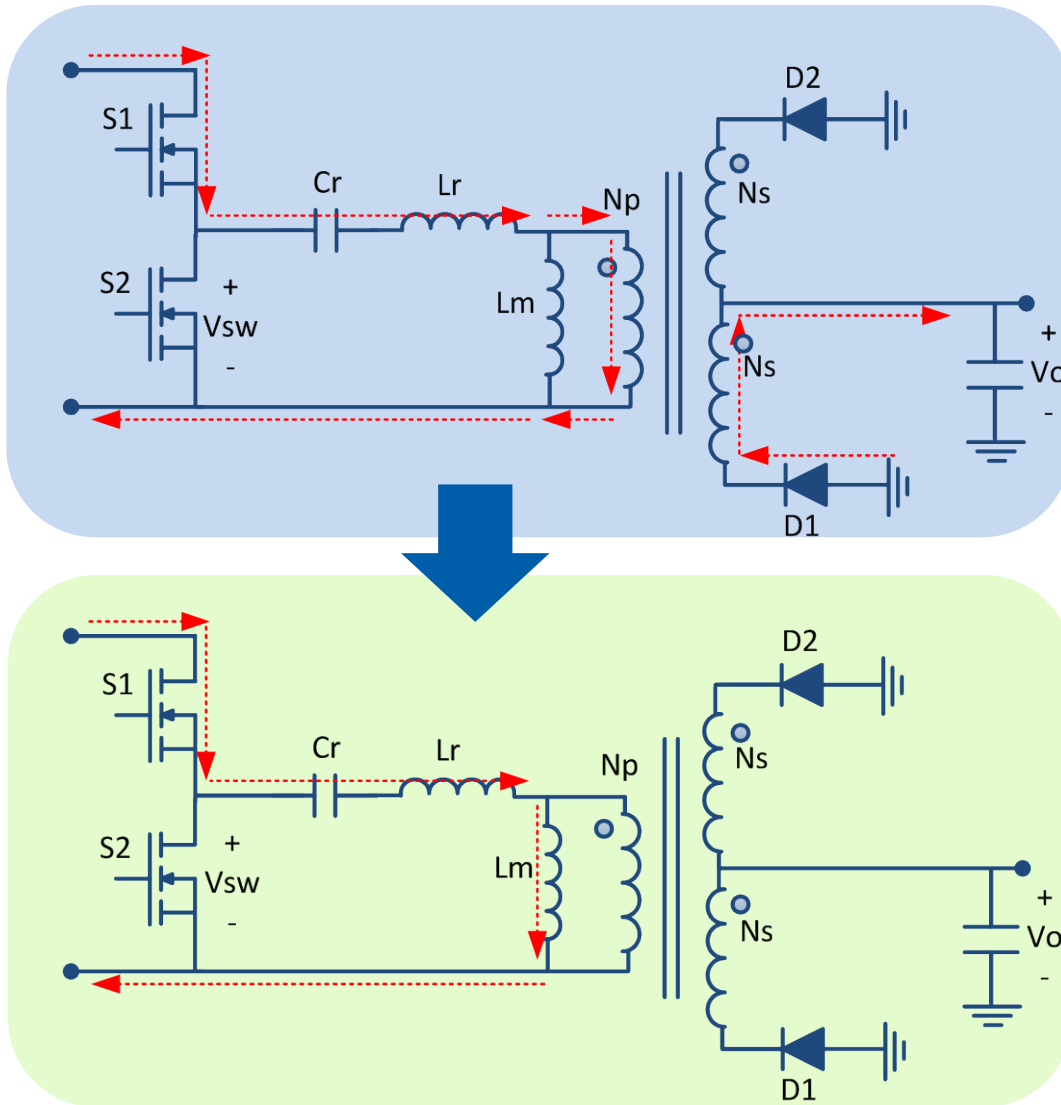


Below Resonance Operation $f_s < f_r$

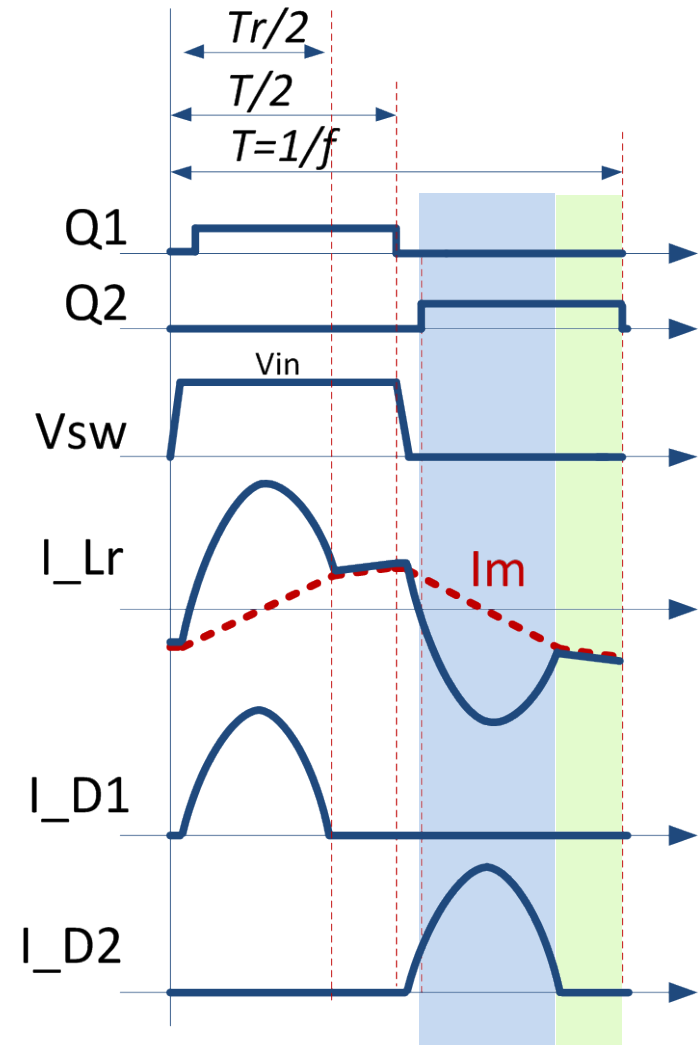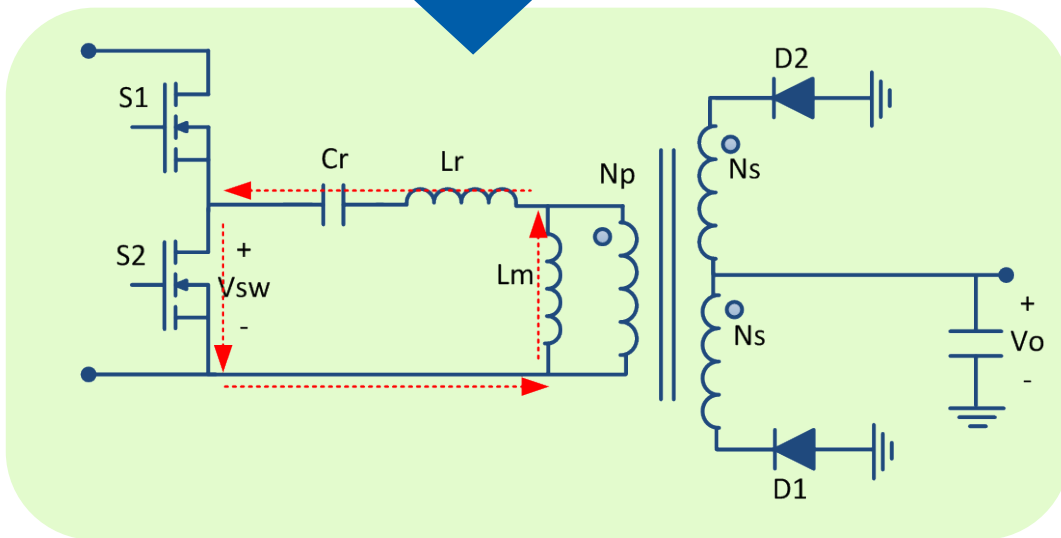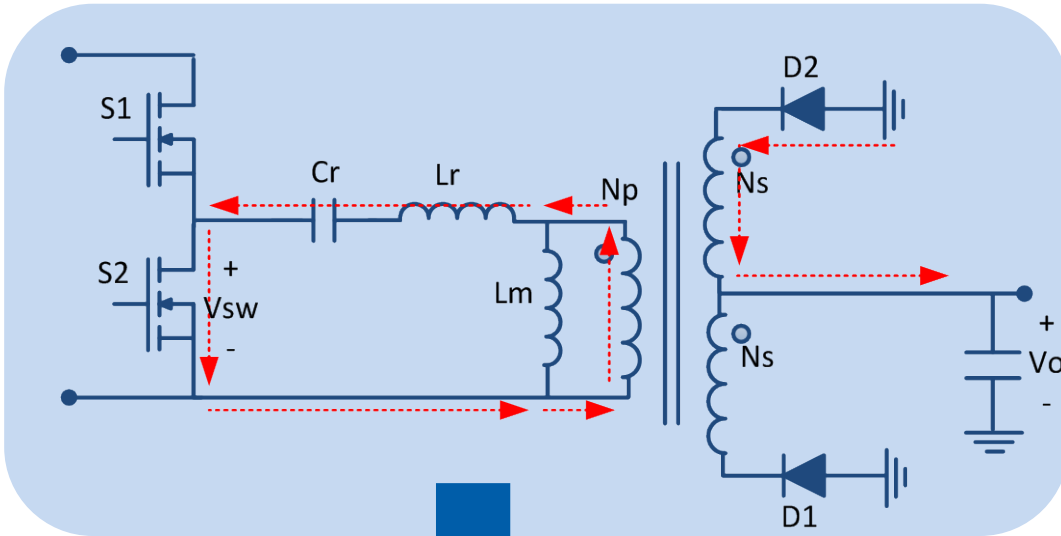

Design Guideline

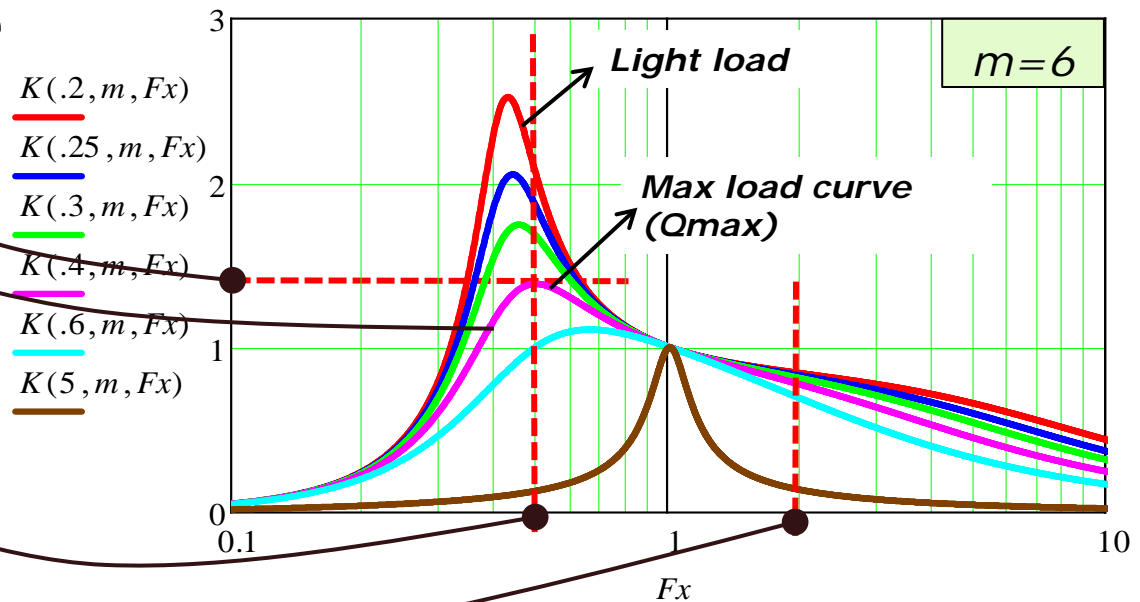- Converter's required maximum voltage gain.
- Find which Q curve have that gain at its peak
- The frequency at that peak is set to be the minimum switching frequency.
- Maximum frequency must be limited for high efficiency, pulse skipping is used for further step down gain.




- Limiting the minimum switching frequency guarantees operating in the inductive region for all load conditions, including and below maximum load.
- Operation beyond maximum load falls into capacitive region (not safe), which is possible during start up and transient conditions → design must allow some safety margin.

Selection of m value

$$m = (L_r + L_m) / L_r$$

- When choosing m , there is a compromise between input voltage range, efficiency, frequency modulation range, soft switching

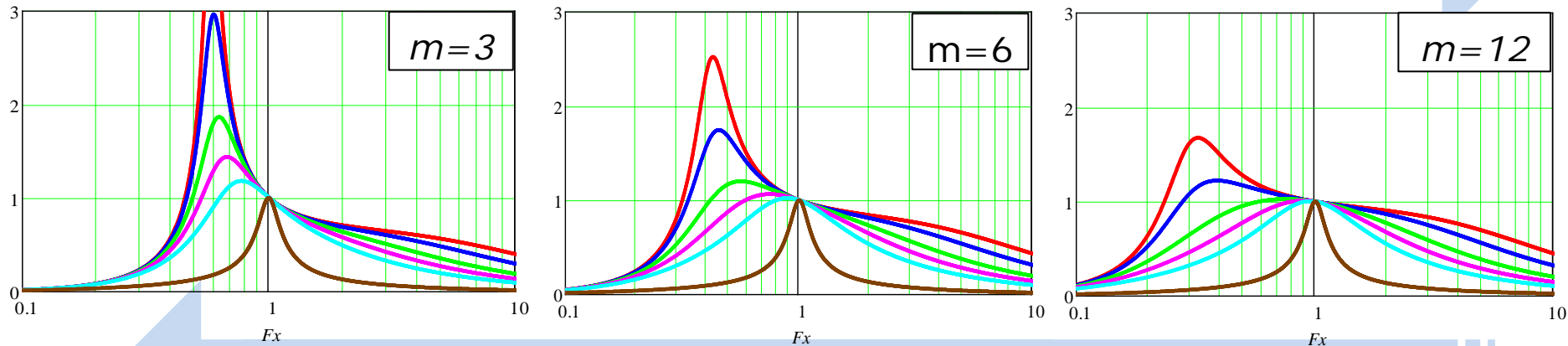Lower magnetizing circulating current → Higher efficiency



Higher boost gain → Wider input range
→ Narrower frequency range


Bridge and Rectifier Selection

Primary Bridge: Half-Bridge compared to Full-Bridge


I_{rms}	I_{rms}^2	# of FETs	FETs conduction losses	N_p	R_{pri}	Transformer primary copper loss
$\times 2$	$\times 4$	$\div 2$	$\times 2$	$\div 2$	$\div 2$	$\times 2$

*Comparison assumes same FET and transformer core

Full-Bridge

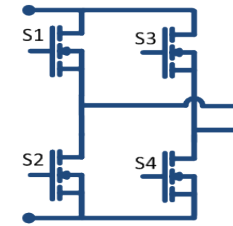

Half-Bridge

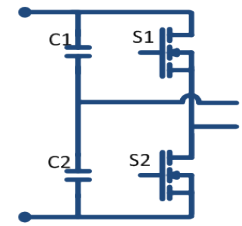


Secondary Rectifier: Full-Wave compared to Full-Bridge


Diode voltage rating	# of diodes	Diode conduction losses	# of secondary windings	R_{sec}	Transformer secondary copper loss
$\times 2$	$\div 2$	$\div 2$	$\times 2$	$\times 2$	$\times 2$

*Comparison assumes same diode drop and transformer core

Full-Bridge

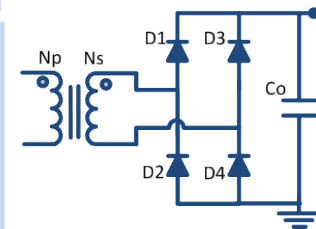

Full-Wave

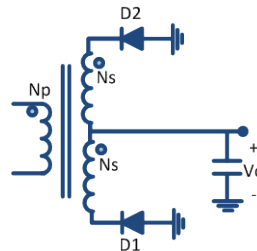

ICE2HS01G


Resonant Mode Controller

Key Features

- Flexible LLC operation
 - Adjustable frequency for Min, Max, OCP and SS → **Easy design**
 - Maximum switching frequency up to 1MHz → **High power density**
 - Adjustable and adaptive dead time control → **Easy design**
- Novel SR operation mode with various protections (***patent pending***)
 - Can be operated at boost region with SR → **Highest achievable efficiency**
 - Variable protections for SR operation → **Easy and Reliable design**
 - Control SR from primary controller → **No need of SR IC, low system cost**
- Accurate setting of switching frequency and dead time
 - **Simple system design**
 - **optimized system efficiency**
- Various protections
 - OTP, OLP, OCP, Latch-off Enable → **Easy system design**


Frequency Oscillator

- FREQ pin is regulated at 2V constantly, the current flowing out from FREQ pin is used to charge the internal oscillator capacitor. The higher output current, the higher switching frequency
- Minimum operation frequency $\rightarrow R_{FMIN}$
- Softstart frequency $\rightarrow R_{FMIN} // R_{OCP} // R_{SS1}$
- Switching frequency during over current protections $\rightarrow R_{FMIN} // R_{OCP}$
- Maximum switching frequency during no load operation $\rightarrow R_{FMIN} // R_{REG}$

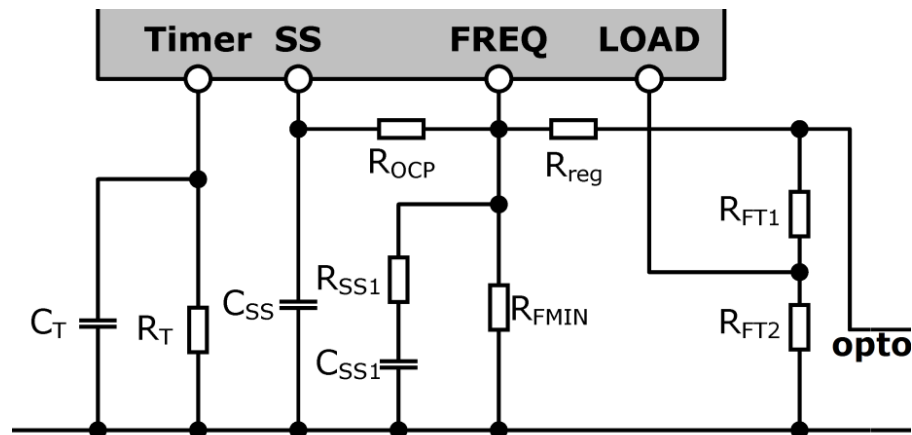

Current Sense and Over Current Protection (OCP)

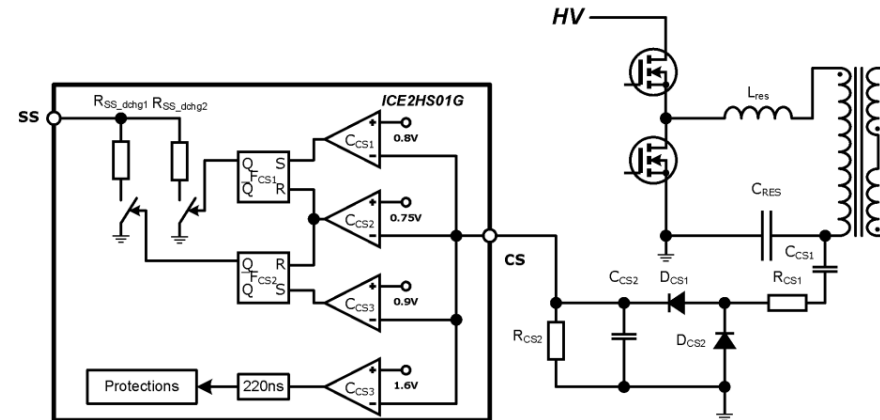- ICE2HS01G increases the switching frequency once an OCP is detected via CS pin
- 3-level OCP protection is implemented
 - Level 1 → switching frequency increase
 - Level 2 → switching frequency rapid increase
 - Level 3 → IC enters into latch protection




SR Control Scheme

- On time prediction and adaptive control
 - Using primary switching frequency, input bus voltage information and preset on time period to determine the on time
 - Using current sensing information for adaptive on time adjustment

-

- Light load is detected when feedback signal is low.
- ICE2HS01G has two options for light load operation
 - High switching frequency as normal operation (disabled burst)
 - Enter into burst mode operation (enabled burst, limited max frequency)

Pin Layout & Typical Application Circuit

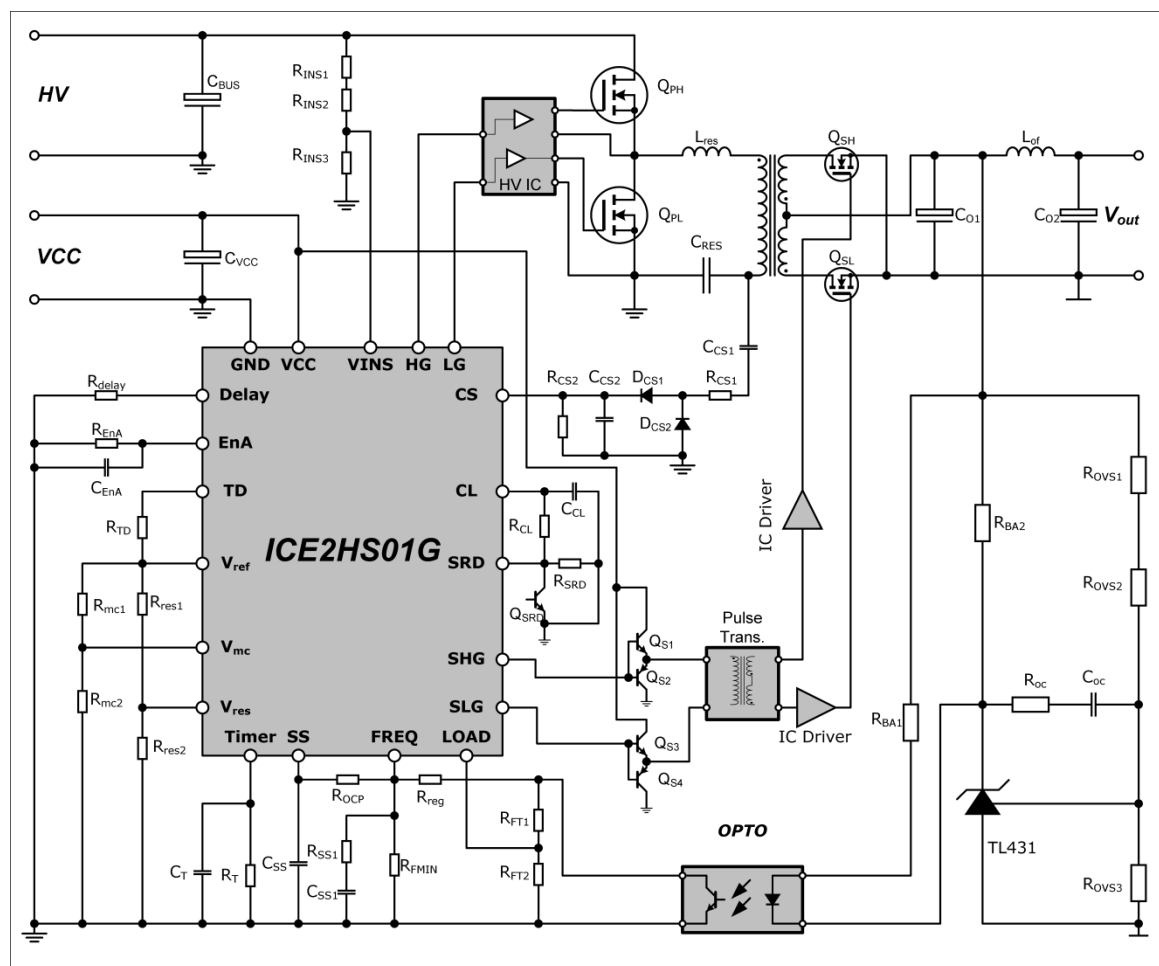

Package → PG-DSO-20-45



Power Management

Pin Number	Pin Name
1	Timer
2	EnA
3	SS
4	LOAD
5	FREQ
6	Delay
7	TD
8	Vmc
9	Vref
10	Vres
11	VINS
12	CS
13	CL
14	SRD
15	GND
16	SLG
17	SHG
18	LG
19	HG
20	VCC

Reference Design #1

Solar Micro-Inverter LLC DC-DC stage

Solar LLC DC-DC stage

Full-Bridge LLC w/ Full-Bridge rectifier


Vo	400V
Vin	16V - 36V
Vin_nom	33V
Po_max	250W @ Vin=36V
Output power derates linearly with input voltage Ex: Output power= 125W @ Vin=18V	
fr	110kHz
fmin	50kHz
fmax	190kHz
Transformer turns ratio	1:12
Cr	0.94uF
Lr	2.3uH
Lm	12.2uH

Bridge FETs

- BSC028N06NS 60V 2.8m Ω
- New Generation
- 55% reduction in Figure of Merit (Qg)
- 37% reduction in Figure of Merit (Qoss)

Rectifier diodes

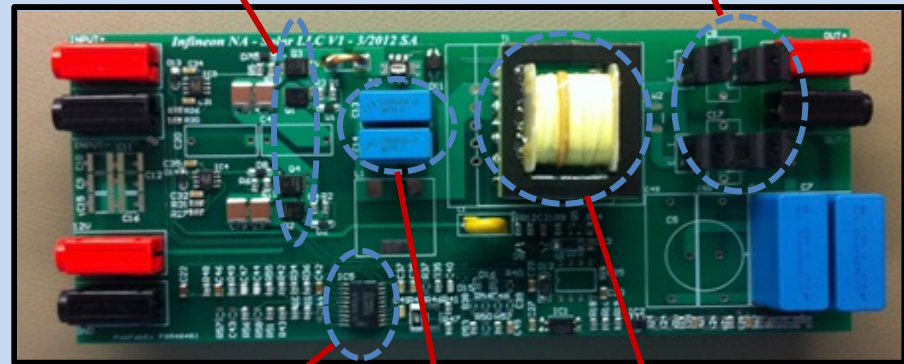- IDH05G65C5 SiC 650V 5A
- Low voltage drop
- Low capacitive charge
- High surge current capability
- Improved thermal performance




LLC analog controller
ICE2HS01G


Resonant capacitor
Film MKP

**Transformer/
Resonant inductor**
E41/17/12

Solar LLC DC-DC stage

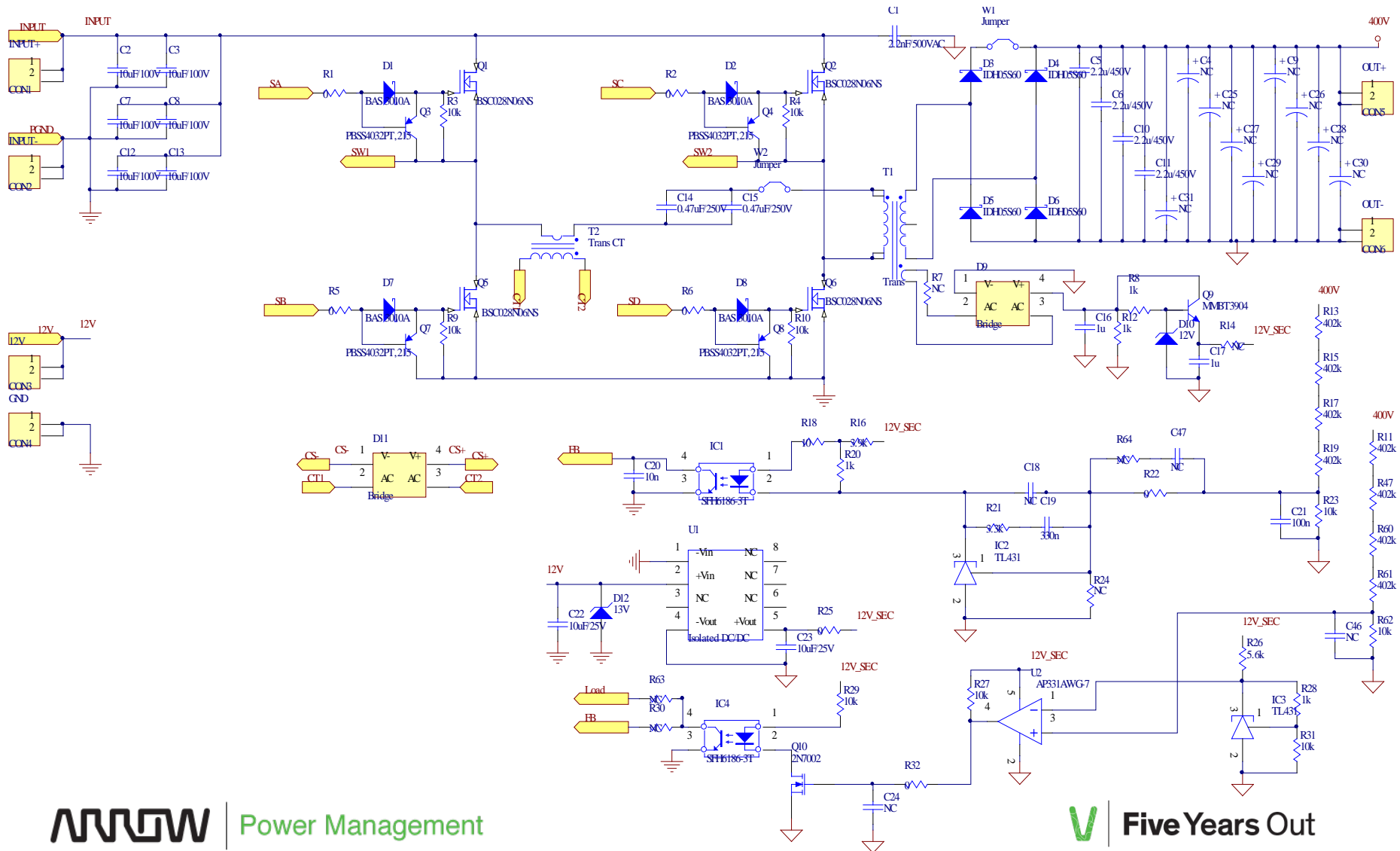


Solar LLC DC-DC stage

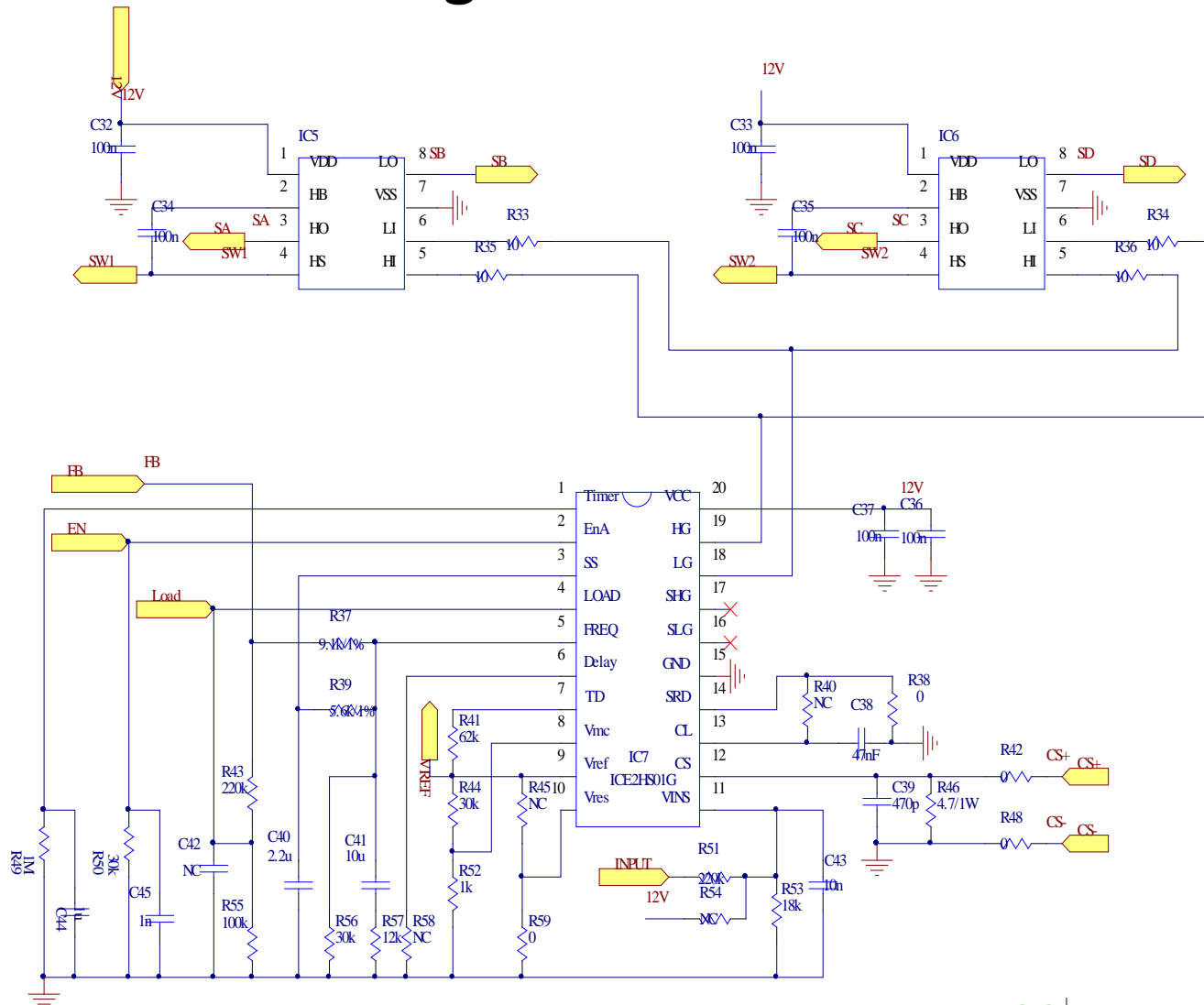

Experimental Waveforms At Resonance Operation $f_s = f_r$

$V_{in} = 33V$

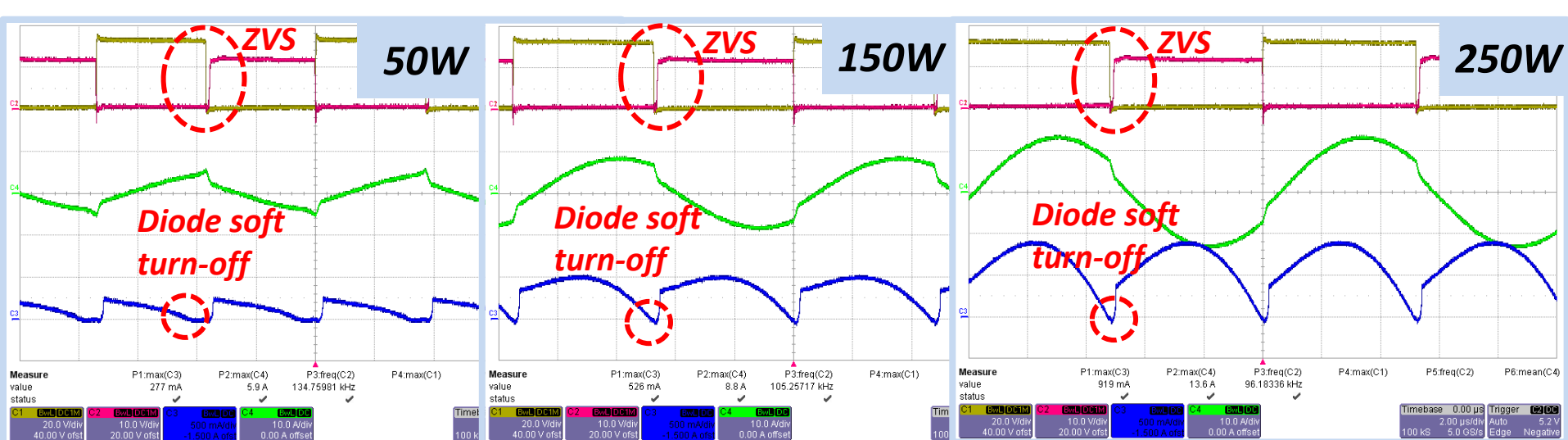


Red: Primary FET V_{gs}
Yellow: Primary FET V_{ds}
Green: Resonant current I_{Lr}
Blue: Rectifier output current $I_{D1} + I_{D3}$


Experimental Waveforms

Below Resonance Operation $f_s < f_r$


$V_{in} = 16V$

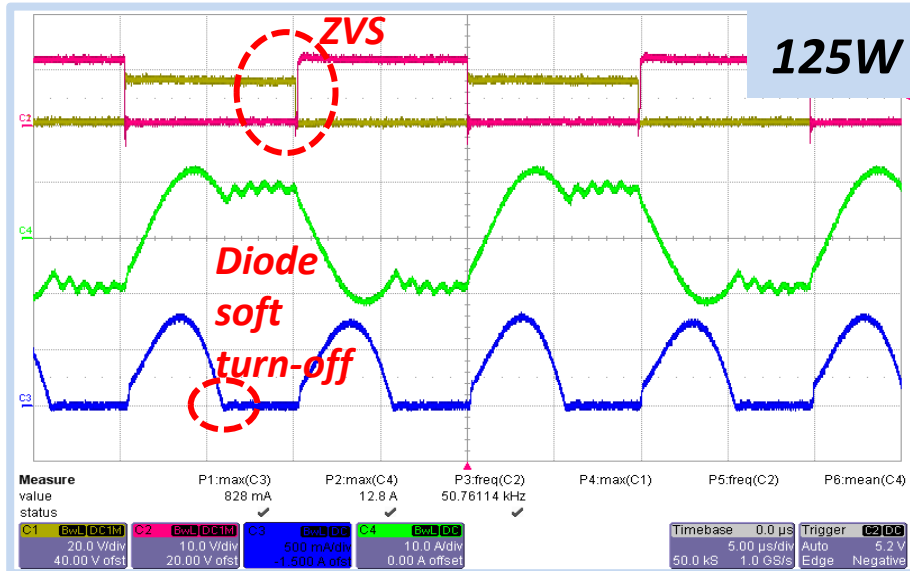


$V_{in} = 24V$

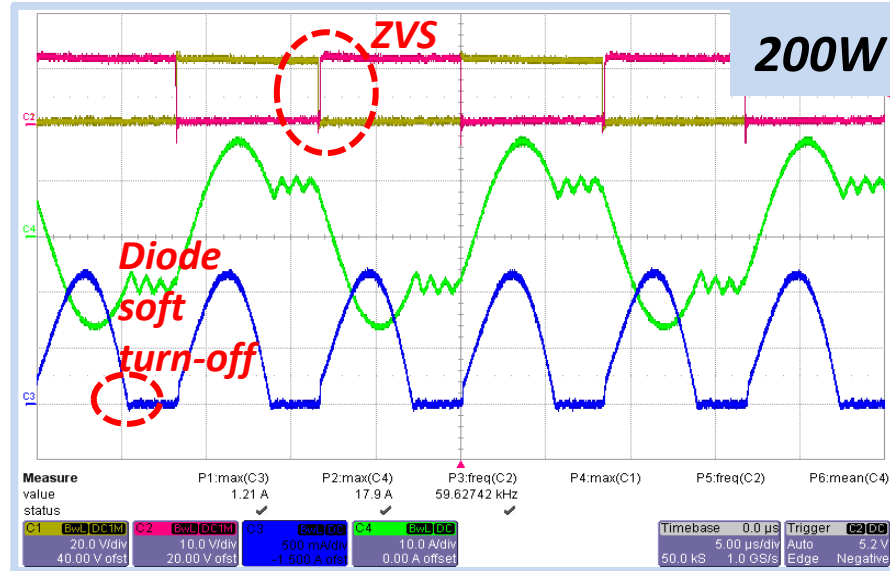

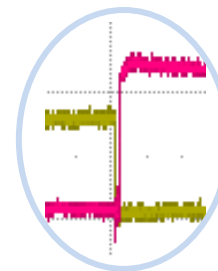Red: Primary FET V_{gs}
Yellow: Primary FET V_{ds}
Green: Resonant current I_{Lr}
Blue: Rectifier output current $I_{D1} + I_{D3}$



ZVS@16V

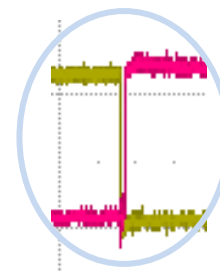

ZVS@24V



Power Management





Five Years Out


Experimental Waveforms

Above Resonance Operation $f_s > f_r$

$V_{in} = 36V$

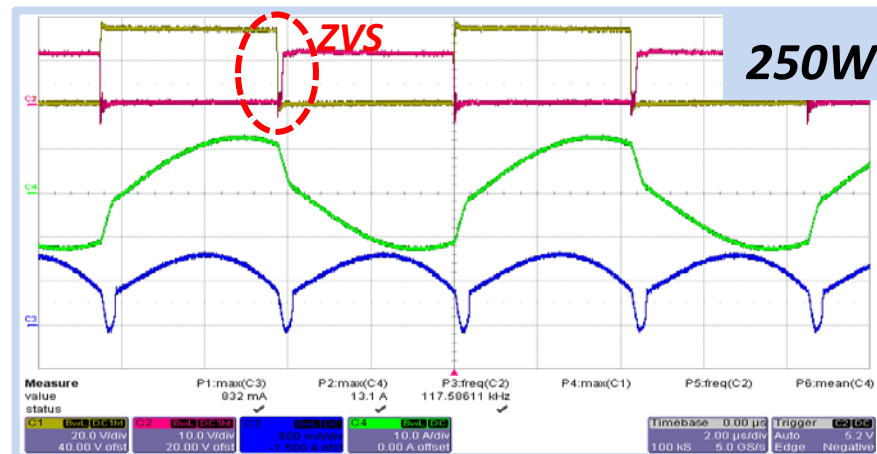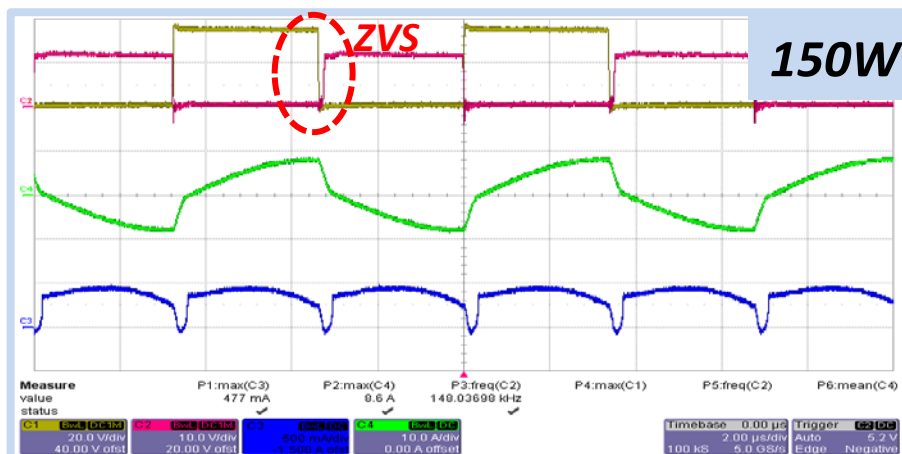

Light Load Missing Cycle Mode

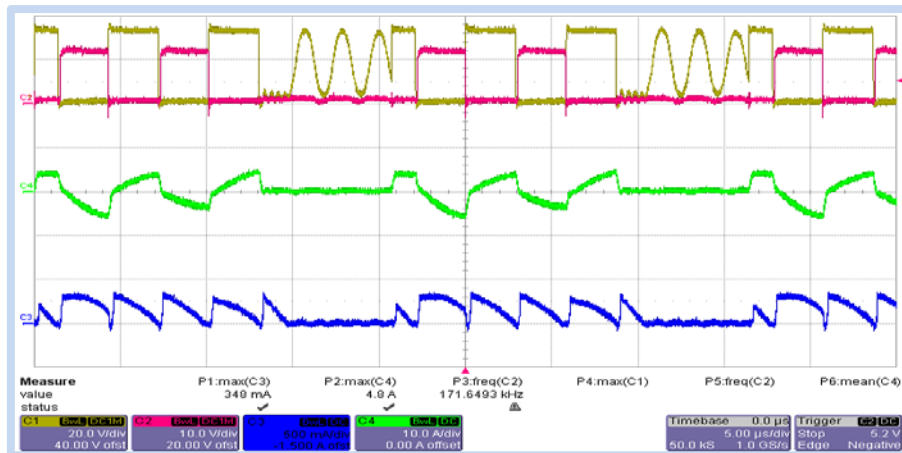

Red: Primary FET V_{gs}

Yellow: Primary FET V_{ds}


Green: Resonant current I_{Lr}

Blue: Rectifier output current $I_{D1} + I_{D3}$

Efficiency

Input Voltage	Output Power (% of 250W)				
	20%	40%	60%	80%	100%
36V	97.1% **	97.1%**	97.1%	97.1%	97.1%
33V	96.0%	97.2%	97.6%	97.6%	97.4%
24V	94.5%	96.8%	97.1%	97.0%	
16V	94.0%	96.3%	96.2%		

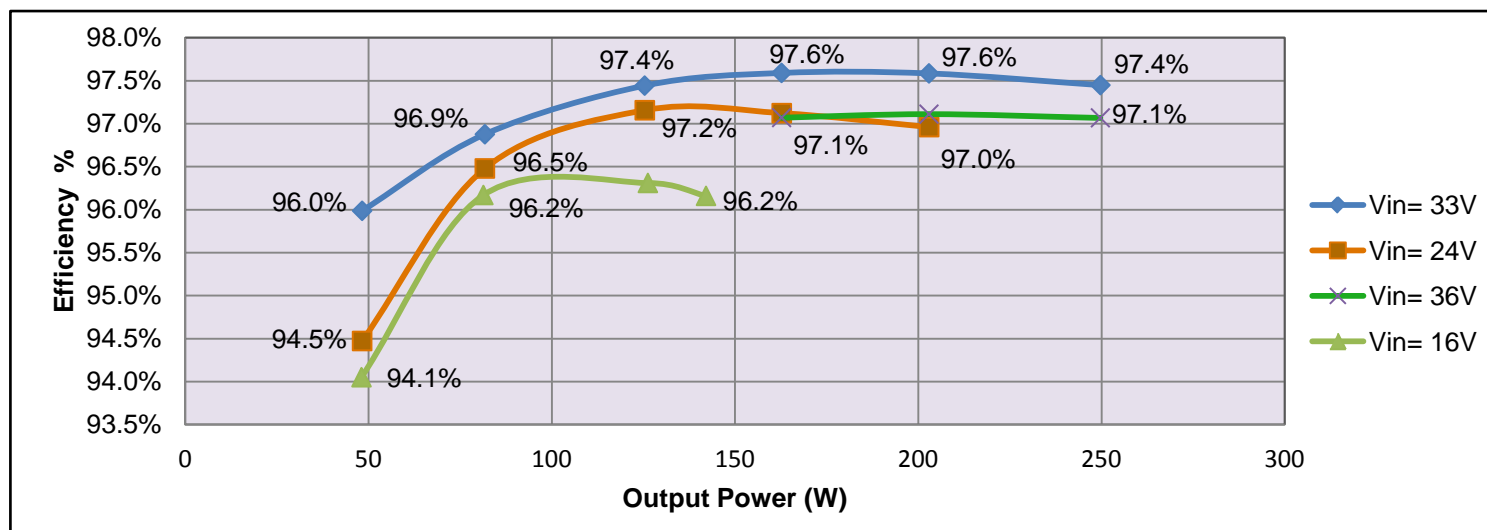**** Missing cycle mode / Burst mode operation**



Reference Design Example #2

SMPS LLC DC-DC stage

SMPS LLC DC-DC stage

Full-Bridge LLC w/ Full-Bridge rectifier

Vo	12V/25A
Vin	315Vdc~420Vdc
Vin_nom	400V
Po_max	300W
fr	85kHz
fmin	30kHz
fmax	180kHz
Transformer turns ratio	16:1
Cr	66nF
Lr	53uH
Lm	690uH



Primary MOSFET: IPA60R199CP


Secondary SR MOSFET: SPP015N04N G

Main Tran.: PQ3230 PC95

Resonant Choke: RM10 PC95


Pulse Tran.: EE13 PC44

SMPS LLC DC-DC stage

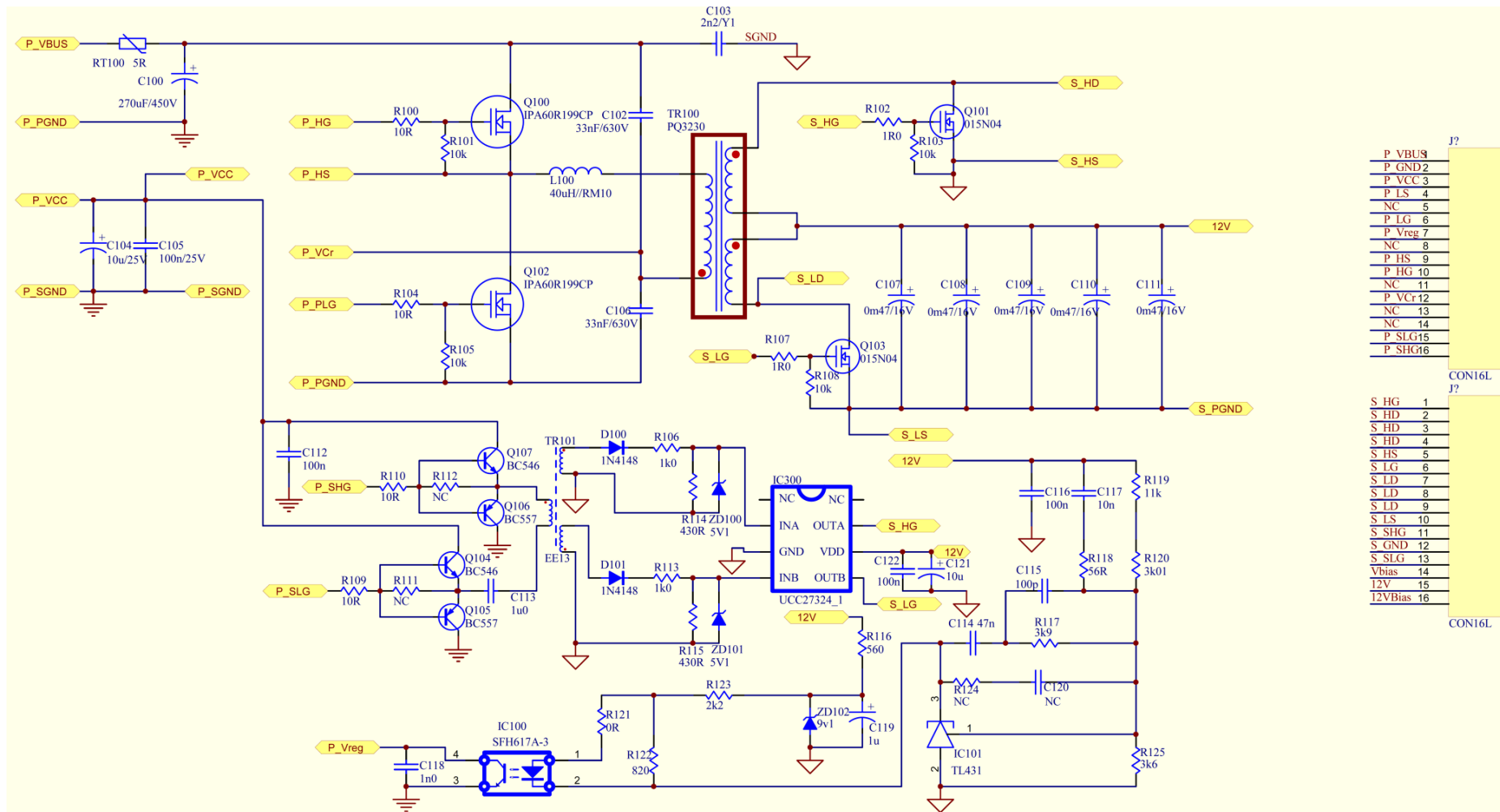


P_VBUS	J?
P_GND2	
P_VCC3	
P_LS4	
NC5	
P_LG6	
P_Vreg7	
NC8	
P_HS9	
P_HG10	
NC11	
P_VCr12	
NC13	
P_SLG15	
P_SHG16	
CON16L	J?
S_HG1	
S_HD2	
S_HD3	
S_HD4	
S_HS5	
S_LG6	
S_LD7	
S_LD8	
S_LD9	
S_LS10	
S_SHG11	
S_GND12	
S_SLG13	
Vbias14	
12V15	
12VBias16	
CON16L	

SMPS LLC DC-DC stage

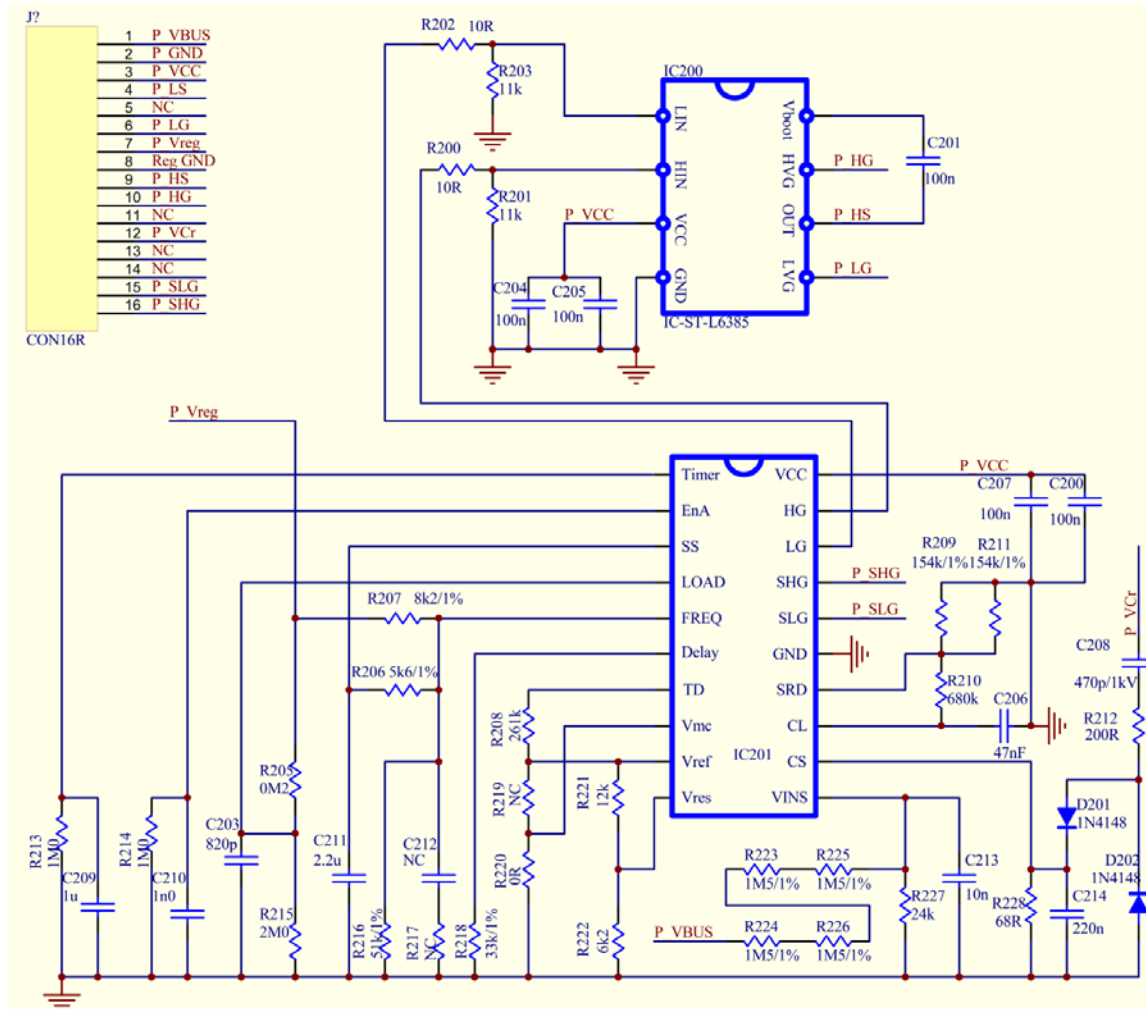


Soft Start

Full load

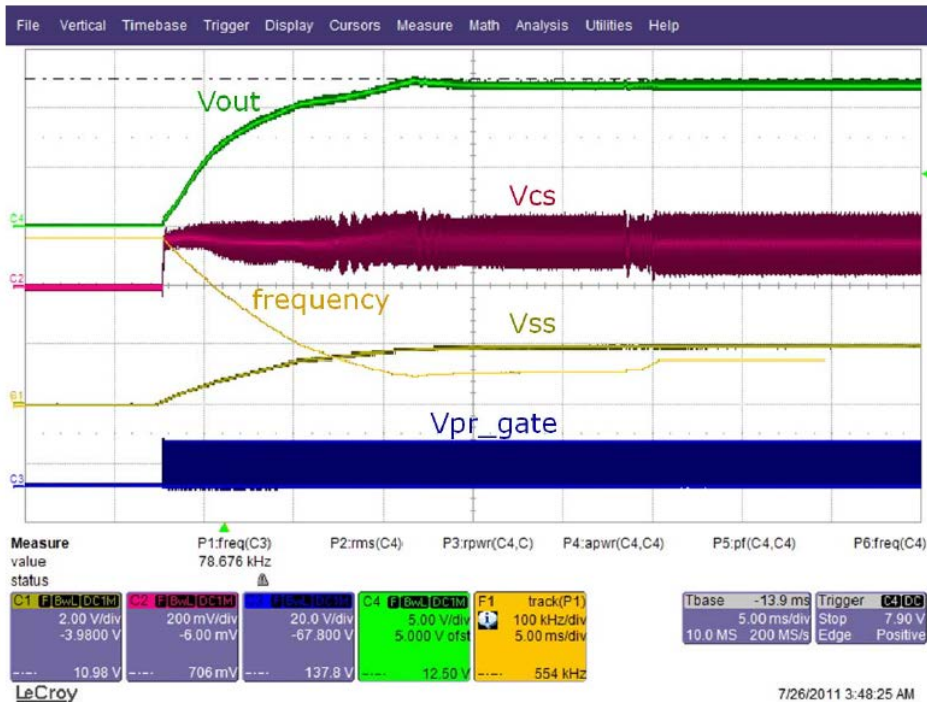

No load

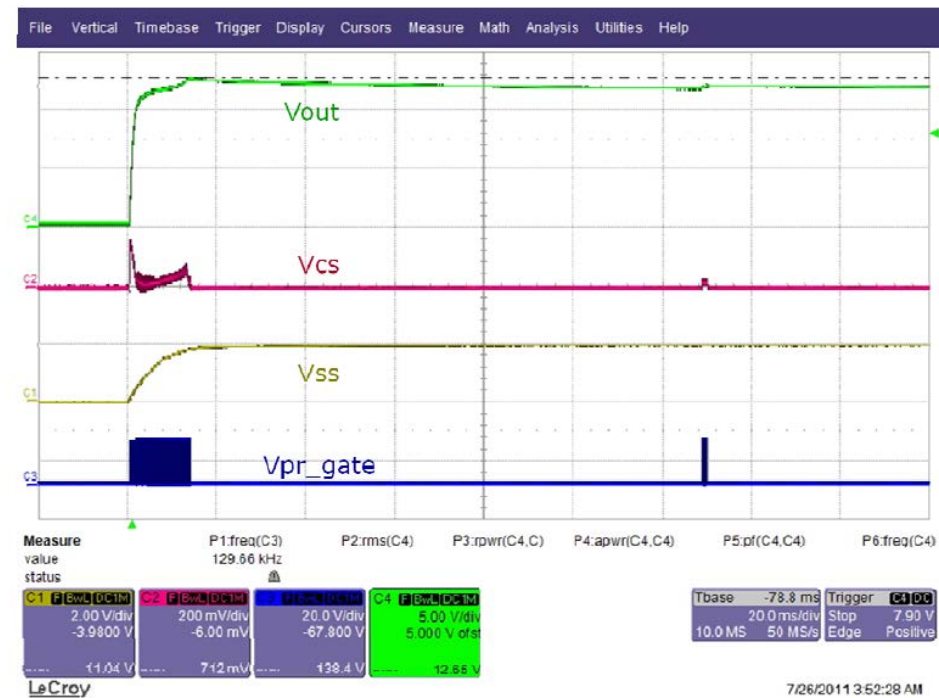


Power Management




Five Years Out

Burst Mode Operation at No Load

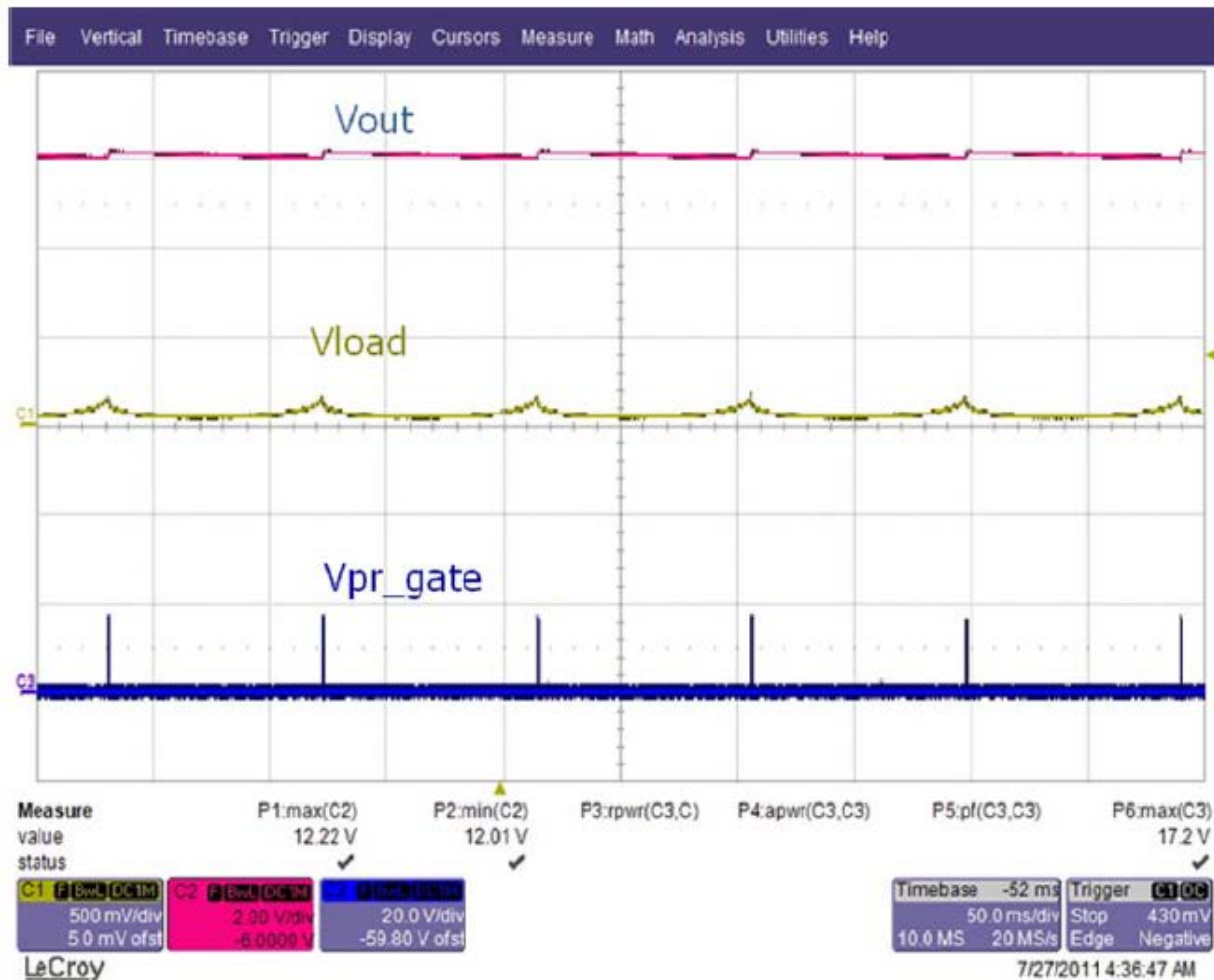


SR Soft Start at Full Load

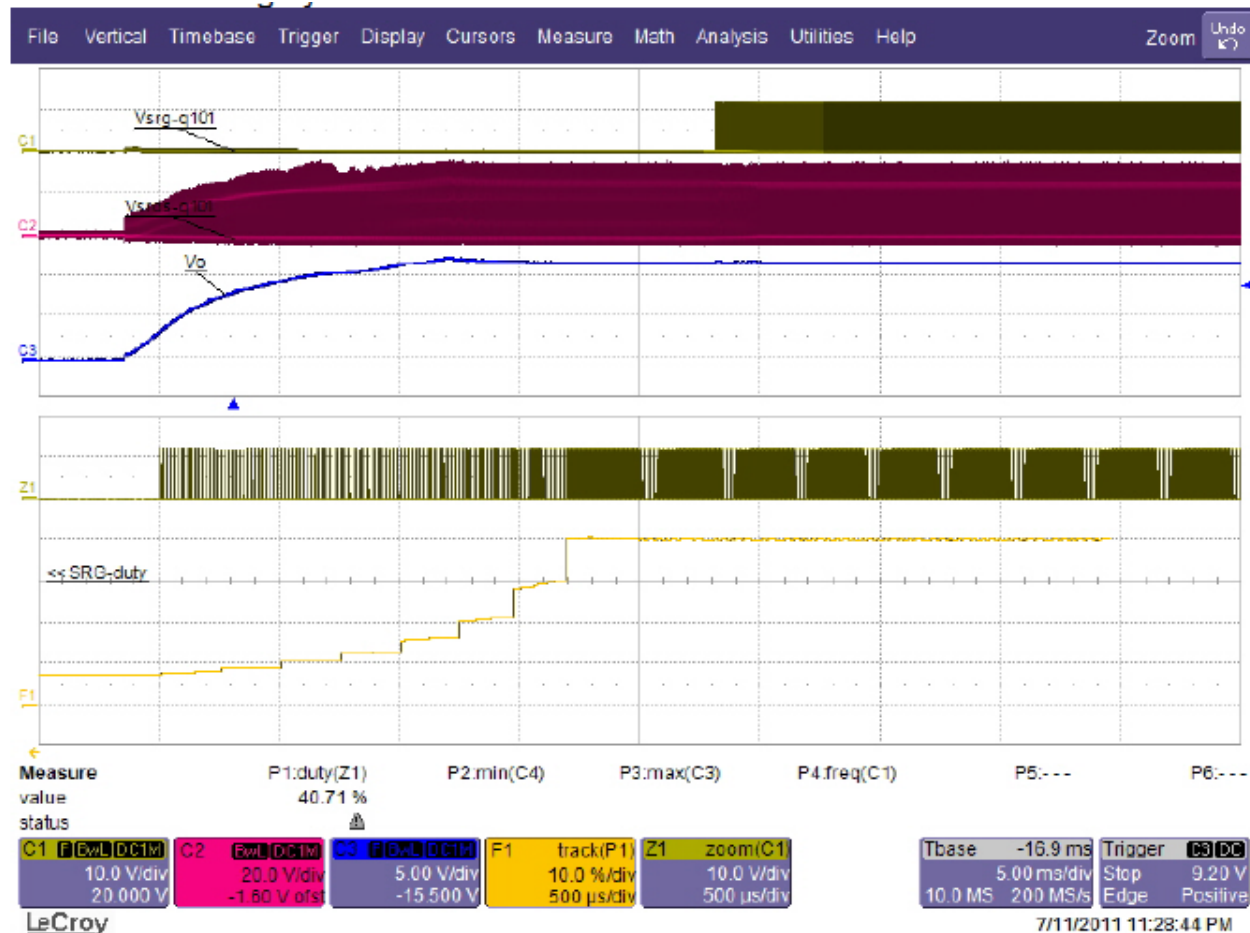

Efficiency

$V_{out}(V)$	$I_{out}(A)$	$P_{out}(W)$	Load(%)	$V_{in}(V)$	$I_{in}(A)$	$P_{in}(W)$	$V_{cc}(V)$	$I_{vcc}(A)$	$P_{vcc}(W)$	Eff.(%)
12.17	1.25	15.21	5%	399.99	0.04	17.06	15.00	0.03	0.375	87.2
12.17	2.49	30.31	10%	399.89	0.08	32.17	15.00	0.03	0.375	93.1
12.17	4.98	60.59	20%	399.77	0.16	62.70	15.00	0.03	0.375	96.1
12.16	12.41	150.95	50%	399.34	0.39	154.46	15.00	0.03	0.375	97.5
12.16	24.87	302.42	101%	399.22	0.78	310.84	15.00	0.03	0.375	97.2

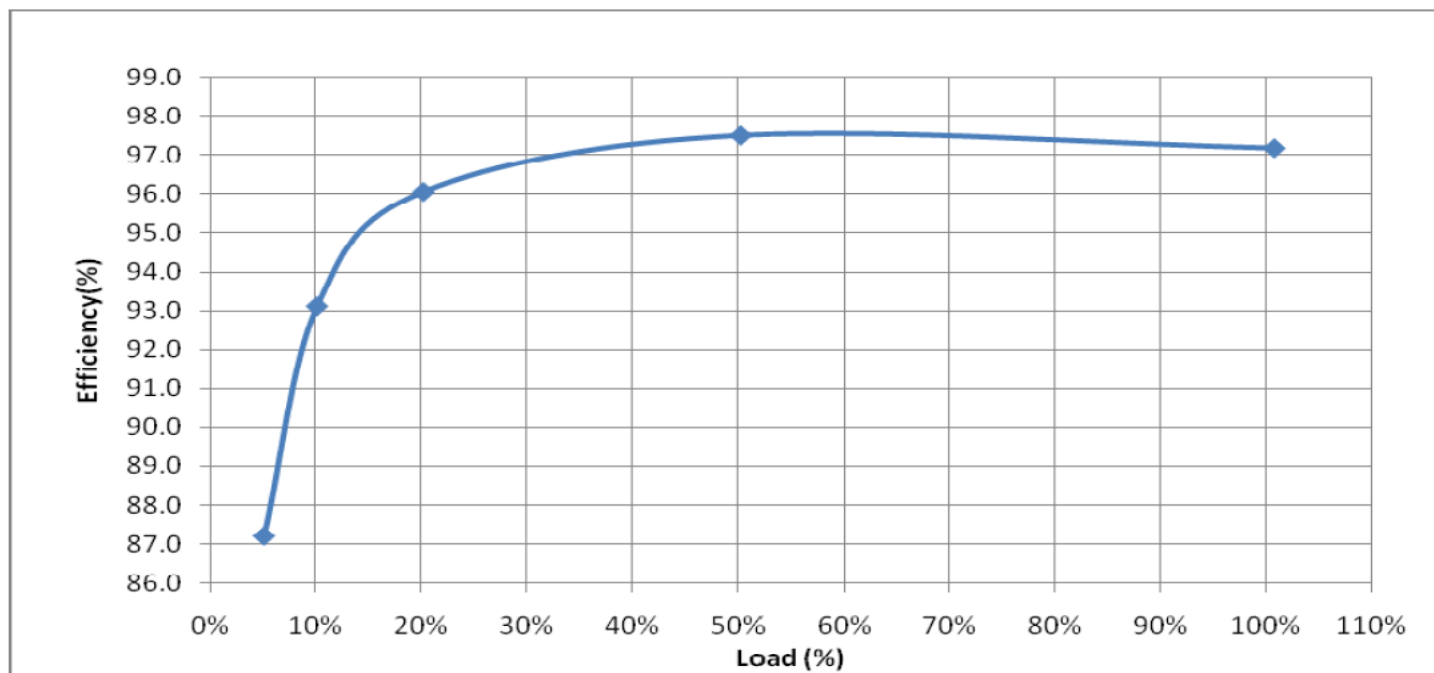

References

1. [300W LLC Evaluation Board with LLC controller ICE2HS01G](#). Application Note.
2. [Resonant LLC Converter: Operation and Design](#). Application Note.
3. [Design Guide for LLC Converter with ICE2HS01G](#). Application Note.
4. [LLC Converter Design Note](#).
5. [High Performance Resonant Mode Controller](#). ICE2HS01G datasheet.

Application Note, V1.1, August 2011

EVAL-2HS01G-300W

300W LLC Evaluation Board with LLC controller ICE2HS01G



Power Management & Supply



Never stop thinking.

Application Note AN-2012-09
V1.0 September 2012



Resonant LLC Converter: Operation and Design 250W 33Vin 400Vout Design Example

Sam Abdel-Rahman
Infineon Technologies North America (IFNA) Corp.



www.infineon.com

Thank You

For More Information:

Existing Arrow Customers: 800 777 2776

New Customers: 800 833 3557

www.arrownac.com/powermanagement